

Digital Logic Circuits

Sources

Lecture Notes

Introduction to Electronics, D Cory, J Freidberg, MIT

Digital Logic Part 1, Part 2, Part 3

<http://www.mit.edu:8001/courses/6.071/lectures/L21.pdf>

<http://www.mit.edu:8001/courses/6.071/lectures/L22.pdf>

<http://www.mit.edu:8001/courses/6.071/lectures/L23.pdf>

Technical Information Sciences 1, B. Blatter, Swiss Federal Institute of Technology

Books

Building Scientific Apparatus, John H Moore, Christopher C. Davis, Michael A Coplan, Perseus Books.

WEB

www.play-hookey.com

<http://www.ee.surrey.ac.uk/Projects/Labview/gatesfunc/>

Boolean Postulates

$$0 \cdot 0 = 0 \qquad 0 + 0 = 0$$

$$1 \cdot 1 = 1 \qquad 1 + 0 = 1$$

$$1 \cdot 0 = 0 \qquad \bar{1} = 0$$

$$1 + 0 = 1 \qquad \bar{0} = 1$$

$$1 + 1 = 1$$

Laws of Boolean Algebra

Communicative

$$A + B = B + A$$

$$A \cdot B = B \cdot A$$

Associative

$$(A + B) + C = A + (B + C)$$

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

Distributive

$$A \cdot (B + C) = A \cdot B + A \cdot C$$

$$A + (B \cdot C) = (A + B) \cdot (A + C)$$

$$(A + B) \cdot (C + D) = A \cdot B + A \cdot D + B \cdot C + B \cdot D$$

de Morgan

$$\overline{A \cdot B \cdot C} = \overline{A} + \overline{B} + \overline{C}$$

$$\overline{A + B + C} = \overline{A} \cdot \overline{B} \cdot \overline{C}$$

Identities

$$A + A = A$$

$$A \cdot A = A$$

$$AB + A\overline{B} = A$$

$$(A + B) \cdot (A + \overline{B}) = A$$

Redundance

$$A + A \cdot B = A$$

$$A + \overline{A} \cdot B = A + B$$

$$\overline{A} + A \cdot B = \overline{A} + B$$

$$A \cdot (A + B) = A$$

$$A \cdot (\overline{A} + B) = A \cdot B$$

$$0 + A = A$$

$$0 \cdot A = 0$$




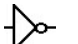




$$1 + A = 1$$

$$1 \cdot A = A$$



$$\overline{A} + A = 1$$

$$\overline{A} \cdot A = 0$$

Logic Gates & Boolean Expression

	OR	$A + B$	
	AND coincide	$A \cdot B$	
	Buffer	A	
	NOT invert	\overline{A}	
	NOR not of quantity A or B	$\overline{A + B}$,	$\overline{A} \cdot \overline{B}$ (not A and not B)
	NAND	$\overline{A \cdot B}$,	$\overline{A} + \overline{B}$
	XOR anti coincide	$A \oplus B$,	$(\overline{A} \cdot B) + (A \cdot \overline{B})$,
	NXOR equivalence	$\overline{A \oplus B}$,	$(A + B) \cdot \overline{A \cdot B}$

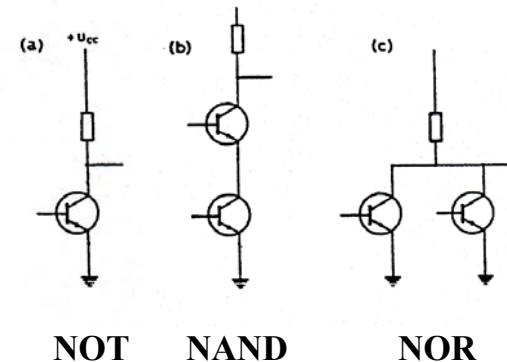 NAND and NOR are universal functions and can be used to construct any of the others.




NOT

NAND


NOR

Logic Gates & Boolean Expression


(a) NOT

 


A	X
0	1
1	0

 


(b) NAND

 


A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

 


(c) NOR

 


A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

 

(d) AND

 


A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

 



 
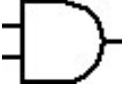
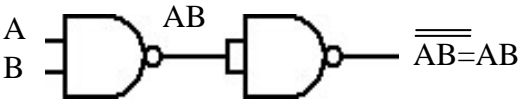
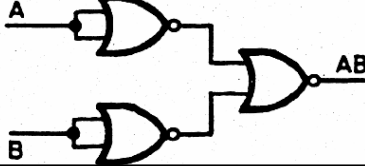



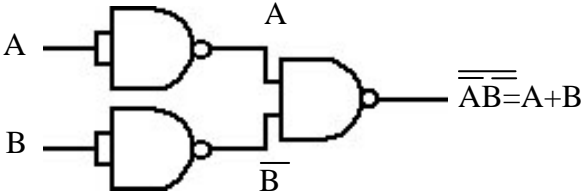
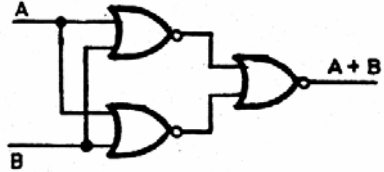
(e) OR



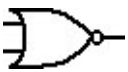
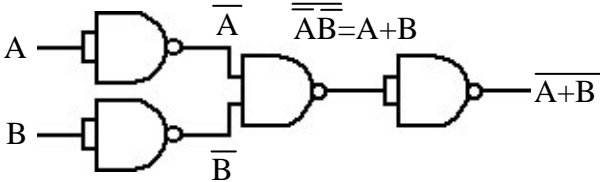

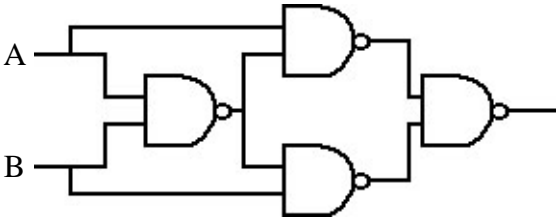

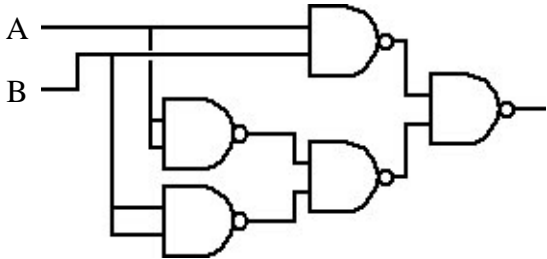
A	B	X
0	0	0
0	1	1
1	0	1
1	1	1



Equivalents (1)

Logic Gate	NAND Equivalent	NOR Equivalent
NOT 	 $\overline{AA} = \overline{A}$	
AND 	 $\overline{\overline{AB}} = AB$	
NAND 		
OR 	 $\overline{\overline{A} \overline{B}} = A+B$	

Equivalents (2)

Logic Gate	NAND Equivalent	NOR Equivalent
<p data-bbox="211 486 287 511">NOR</p> 	 <p data-bbox="1011 472 1138 511">$\overline{A} \quad \overline{B}$ $\overline{\overline{A} \overline{B}} = A+B$</p>	
<p data-bbox="211 722 287 746">XOR</p> 		
<p data-bbox="211 1001 306 1025">XNOR</p> 		

Binary Adder

Adding: Adding binary numbers is just like adding decimal numbers; whenever the result of adding one column of numbers is greater than one digit, a 1 is carried over to the next column to be added.

Example:

$$\begin{array}{r}
 20_{10} = 000 \overset{1}{\mid} 10 \overset{1}{\mid} 100 \\
 87_{10} = 010 \mid 10 \mid 111 \\
 \hline
 011 \mid 01 \mid 011
 \end{array}$$


Subtraction: This operation is similar to decimal subtraction. The only potential point of confusion is that when “borrowing” from one column a $10_2 (=2_{10})$ is carried over (not just a 1) to the next column. A trick to subtracting binary numbers is to add the 2’s complement of the subtracting number to the true binary representation of the number from which it is subtracting.

Example:

$$\begin{array}{r}
 +19_{10} = 00010011 \\
 -7_{10} = 11111001 \\
 \hline
 \text{Sum} = 00001100
 \end{array}$$

States of Binary Adder

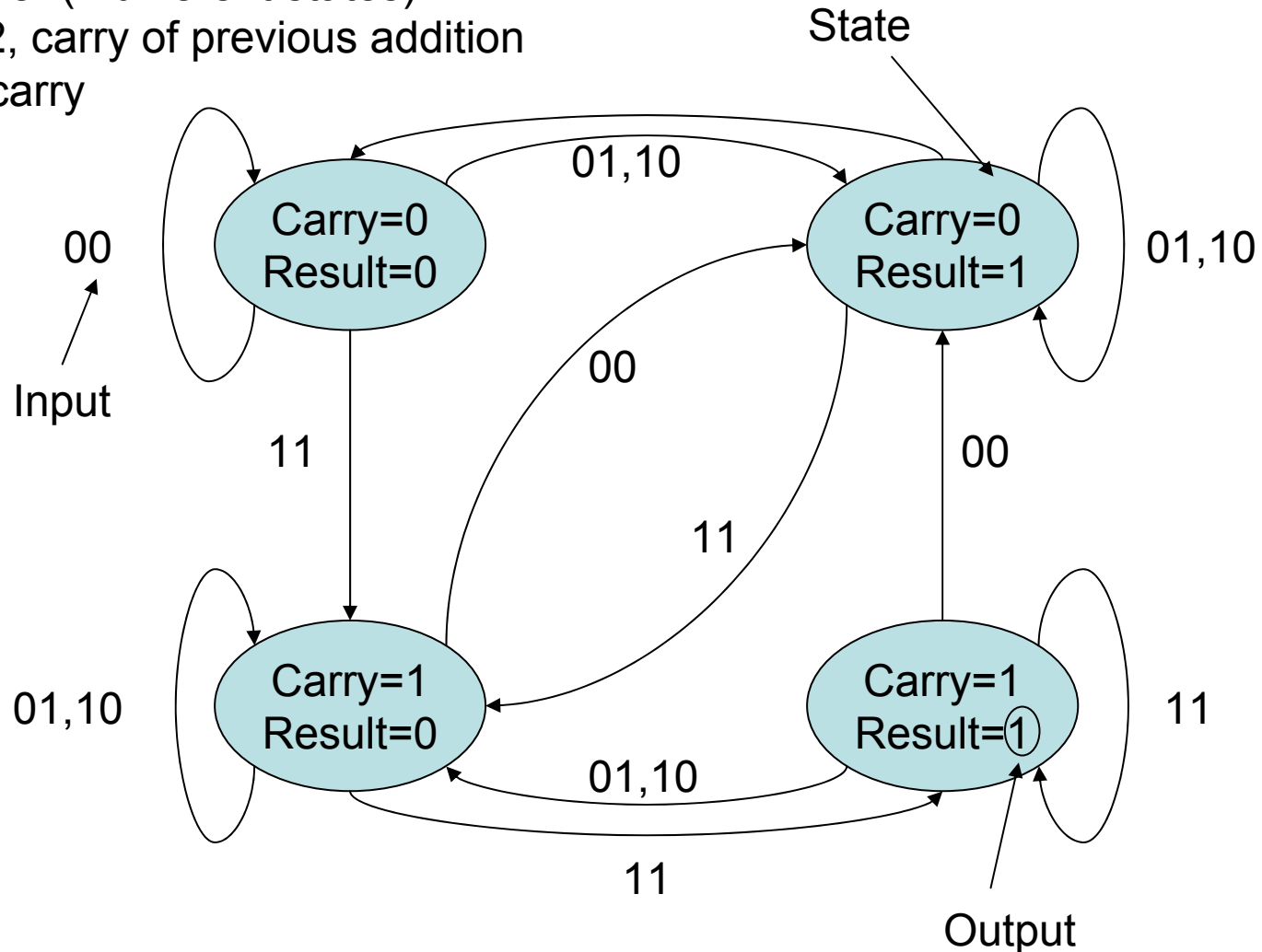Binary Adder (4 different states)
input x1,x2, carry of previous addition
output: y, carry




Logical Expression

Input			Output		Min		Max	
x_1	x_2	c_i	y	c_{i+1}	y	c_{i+1}	y	c_{i+1}
0	0	0	0	0			$x_1+x_2+c_i$	$x_1+x_2+c_i$
0	0	1	1	0	$\bar{x}_1\bar{x}_2c_i$			$x_1+x_2+\bar{c}_i$
0	1	0	1	0	$\bar{x}_1x_2\bar{c}_i$			$x_1+\bar{x}_2+c_i$
0	1	1	0	1		$\bar{x}_1x_2c_i$	$x_1+\bar{x}_2+\bar{c}_i$	
1	0	0	1	0	$x_1\bar{x}_2\bar{c}_i$			$\bar{x}_1+x_2+c_i$
1	0	1	0	1		$x_1\bar{x}_2c_i$	$\bar{x}_1+x_2+\bar{c}_i$	
1	1	0	0	1		$x_1x_2\bar{c}_i$	$\bar{x}_1+\bar{x}_2+c_i$	
1	1	1	1	1	$x_1x_2c_i$	$x_1x_2c_i$		


$$y = \bar{x}_1\bar{x}_2c_i + \bar{x}_1x_2\bar{c}_i + x_1\bar{x}_2\bar{c}_i + x_1x_2c_i$$

$$c_{i+1} = \bar{x}_1x_2c_i + x_1\bar{x}_2c_i + x_1x_2\bar{c}_i + x_1x_2c_i$$


Circuit

 


Half Adder

 

Alternative Representation

 


Half-adder symbol

 


These circuits add two one-bit numbers and produce one two-bit number with a carry.

Full Adder


Full-Adder:

 

full-adder symbol

 


Full Adder Implementation

 


4bit Adder

Now, with the half-adders and full-adders, a multi-bit adder can be constructed:



4-bit Adder:

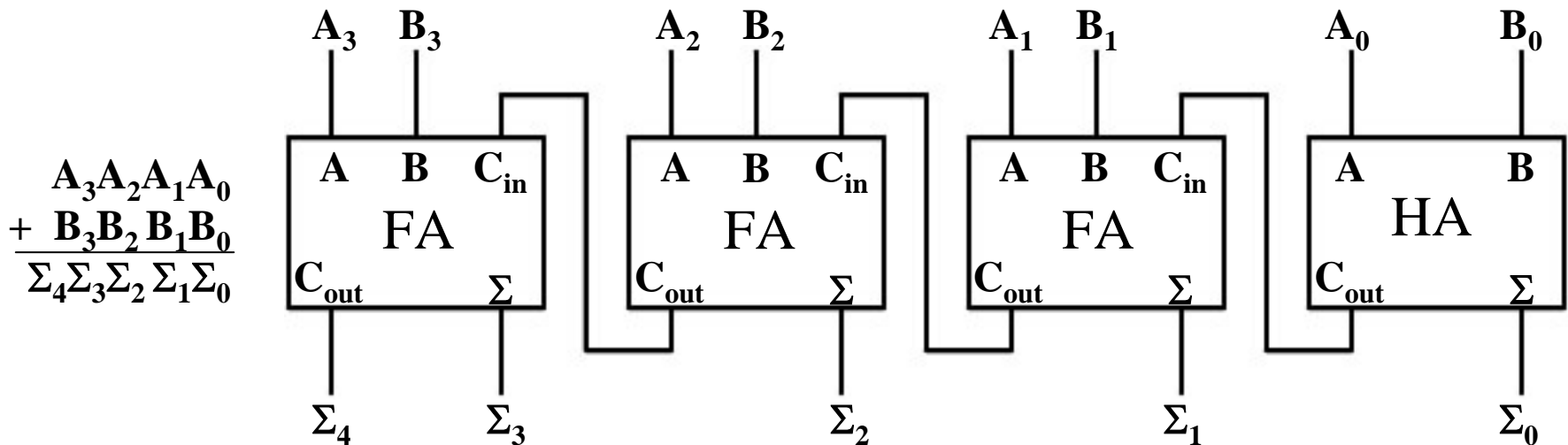

Adder / Subtractor

 


Decoder

  


Encoder

 Only one of the input lines is allowed to be active.
N input lines to $\log_2(N)$ output lines.




Encoder Example

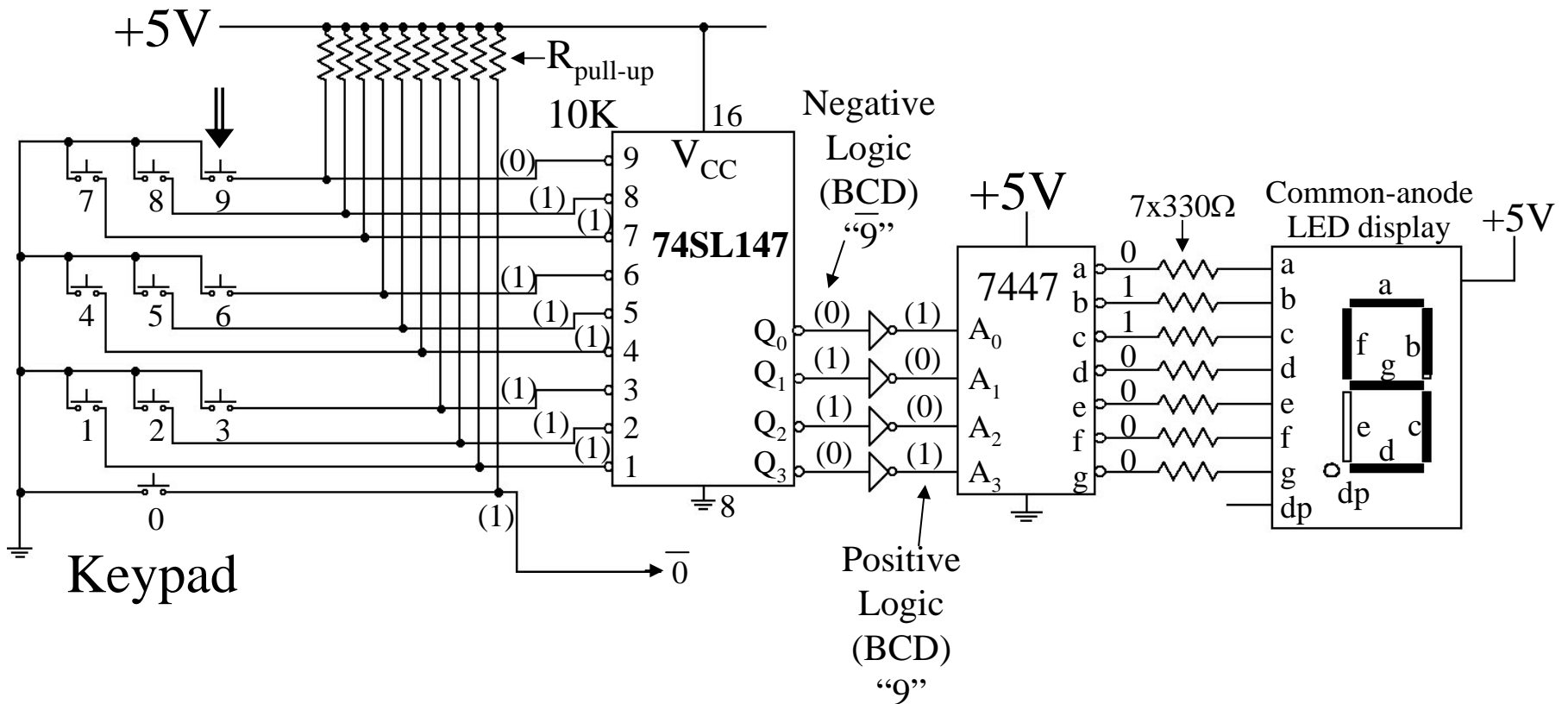

Arithmetic Logical Units

 - Shift Register (Division or Multiplication by 2)




Example: X: 0110 0111

$f=1$ Division Y = 0011 0011

$f=0$ Multiplication Y = 1100 1110

Arithmetic Logical Units


- General ALU

 

A, B: input
 f_i : select arithmetical function
 Z_i : state indicator of ALU,
e.g. negative, carry,
normally transmitted into
condition code register

Arithmetic Logical Units

- Example simple ALU

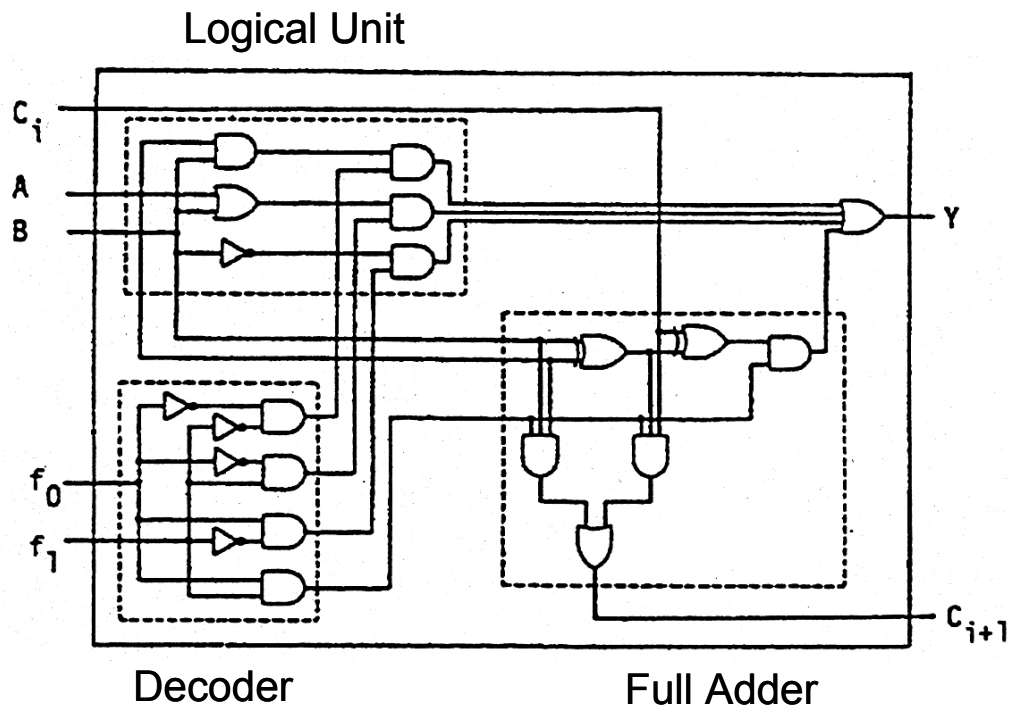

Selected function:

f_0 f_1 function

0 0 $A*B$

0 1 $A+B$

1 0 not B

1 1 $A+B+C_i$ with carry